

SUBJECT :

TOPIC:


TIME:

DATE:

1. (b)


2. (c)

3. (a)

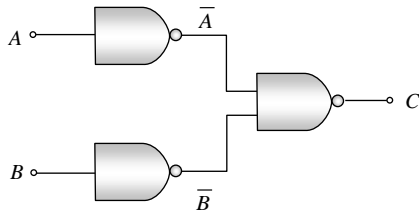

$$C = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A+B}} = A+B \text{ (De Morgan's theorem)}$$

Hence output C is equivalent to OR gate.

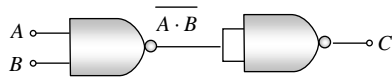

$$C = \overline{\overline{AB} \cdot \overline{B}} = \overline{\overline{AB+B}} = AB+AB = AB$$

In this case output C is equivalent to AND gate.

4. (b) In 'NOR' gate $Y = \overline{A+B}$
i.e. $\overline{0+0} = \overline{0} = 1$, $\overline{1+0} = \overline{1} = 0$
 $\overline{0+1} = \overline{1} = 0$, $\overline{1+1} = \overline{1} = 0$

5. (c) For 'XNOR' gate $Y = \overline{A} \overline{B} + AB$
i.e. $\overline{0} \cdot \overline{0} + 0 \cdot 0 = 1 \cdot 1 + 0 \cdot 0 = 1 + 0 = 1$
 $\overline{0} \cdot \overline{1} + 0 \cdot 1 = 1 \cdot 0 + 0 \cdot 1 = 0 + 0 = 0$
 $\overline{1} \cdot \overline{0} + 1 \cdot 0 = 0 \cdot 1 + 1 \cdot 0 = 0 + 0 = 0$
 $\overline{1} \cdot \overline{1} + 1 \cdot 1 = 0 \cdot 0 + 1 \cdot 1 = 0 + 1 = 1$

6. (a) The Boolean expression for 'NOR' gate is
 $Y = \overline{A+B}$
i.e. if $A=B=0$ (Low), $Y = \overline{0+0} = \overline{0} = 1$ (High)

7. (a)

8. (d) The Boolean expression for 'AND' gate is $R = P \cdot Q$
 $\Rightarrow 1 \cdot 1 = 1$, $1 \cdot 0 = 0$, $0 \cdot 1 = 0$, $0 \cdot 0 = 0$

9. (c) For 'NAND' gate (option c), output = $\overline{0 \cdot 1} = \overline{0} = 1$

10. (a) AND + NOT \rightarrow NAND

11. (c) For 'NOT' gate $X = \overline{A}$


12. (b) For 'AND' gate, if output is 1 then both inputs must be 1.

13. (b)

14. (a)

15. (a) The given symbol is of 'AND' gate.

16. (b)

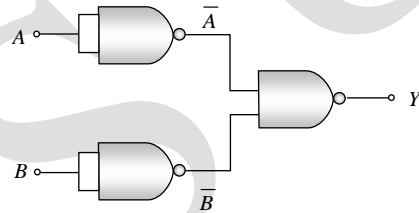

$$Y = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A+B}} = A+B$$


This output equation is equivalent to OR gate.

17. (c) If inputs are A and B then output for NAND gate is
 $Y = \overline{AB}$

$$\Rightarrow \text{If } A=B=1, Y = \overline{1 \cdot 1} = \overline{1} = 0$$

18. (b)

19. (c)

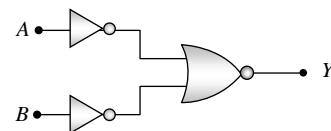

$$Y = \overline{\overline{A+B}}$$

According to De Morgan's theorem

$$Y = \overline{\overline{A+B}} = \overline{\overline{A} \cdot \overline{B}} = A \cdot B$$

This is the output equation of 'AND' gate.

20. (a) The given symbol is of NAND gate.